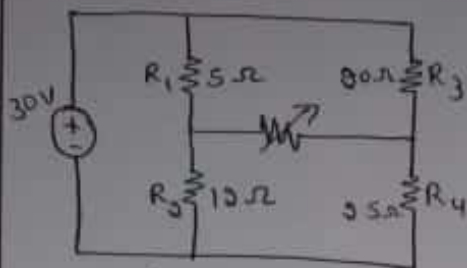


# Circuit challenge [Simulation]

VATHSALAK.S  
4AL18EC057

→ Max. power transfer:-



Disconnected the load resistance from the load terminals a & b. To represent the given ckt as thevenin's equivalent. we have to determine  $V_{TH}$  &  $R_{TH}$ .

The thevenin's voltage @ voltage across the terminal AB is  $V_{AB} = V_A - V_B$

$$V_A = V \times \frac{R_2}{(R_1 + R_2)} = 30 \times \frac{12}{(5 + 12)}$$

$$V_A = 21.7 \text{ V}$$

$$V_B = V \times \frac{R_4}{(R_3 + R_4)} = 30 \times \frac{25}{(20 + 25)}$$

$$V_B = 16.66 \text{ V}$$

$$\therefore V_{TH} = V_{AB} = V_A - V_B = 4.51 \text{ V}$$

To calculate  $R_{TH}$ : By replacing source with their internal resistance.

$$R_{TH} = R_{AB} \cdot \left( \frac{R_1 R_2}{R_1 + R_2} \right) + \left( \frac{R_3 R_4}{R_3 + R_4} \right)$$



$$R_{TH} = 14.64 \Omega$$

$$\text{where } R_L = R_{TH} = 14.64 \Omega$$

And the max. power transferred  $V_{TH}$  to load  $R_L$  is,

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{(4.51)^2}{4 \times 14.64}$$

$$= 343.3 \text{ mW}$$

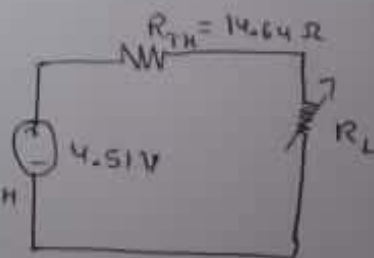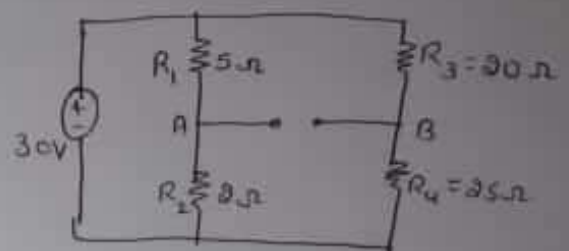

DC

P(RL)

347.3  
mW

+ Add Expression

Export Results

Run DC Solver

DC Sweep

Time Domain

Frequency Domain

